 


## Question

Q.39 The Boolean function realized by the logic circuit shown is



(A)  $F = \sum m(0, 1, 3, 5, 9, 10, 14)$

(B)  $F = \sum m(2, 3, 5, 7, 8, 12, 13)$

(C)  $F = \sum m(1, 2, 4, 5, 11, 14, 15)$

(D)  $F = \sum m(2, 3, 5, 7, 8, 9, 12)$

# Implementation of 4x1 Multiplexer using Verilog and Vaman Board

## Hardware Implementation Report

### Q.1 FPGA Experiment

#### Objective

To design, simulate, and physically implement a 4x1 multiplexer using Verilog HDL on a Vaman FPGA development board. The output of the multiplexer is observed using LEDs.

#### Hardware Required

- Vaman FPGA Board
- LEDs
- Resistors (220  $\Omega$ )
- Jumper Wires
- Breadboard

#### Theory

A multiplexer (MUX) is a combinational circuit that selects one of several input signals and forwards the selected input to a single output line. A 4x1 multiplexer has 4 input lines, 2 selection lines, and 1 output line.

The truth table for a 4x1 MUX is as follows:

Select Lines (S1 S0)	Selected Input	Output (Y)
00	I0	I0
01	I1	I1
10	I2	I2
11	I3	I3

## Verilog Code

```

1 module mux4x1(
2     input I0, I1, I2, I3,
3     input S0, S1,
4     output reg Y
5 );
6 always @(*) begin
7     case ({S1, S0})
8         2'b00: Y = I0;
9         2'b01: Y = I1;
10        2'b10: Y = I2;
11        2'b11: Y = I3;
12    endcase
13 end
14 endmodule

```

Listing 1: 4x1 Multiplexer Verilog Code

## PCF File (Pin Constraint File)

```

1 set_io I0 J15 # Switch 1
2 set_io I1 L16 # Switch 2
3 set_io I2 M13 # Switch 3
4 set_io I3 R15 # Switch 4
5 set_io S0 P14 # Select Line 1
6 set_io S1 N16 # Select Line 2
7 set_io Y K13 # LED Output

```

Listing 2: .pcf File for Vaman Board Pin Mapping

## Procedure

1. Write the Verilog code for a 4x1 multiplexer.
2. Create a new project in the Vaman IDE or through command line using Yosys and nextpnr.
3. Add the Verilog file and PCF file to the project.
4. Synthesize and implement the design.
5. Generate the bitstream or binary (.bin) file.

6. Upload the bitstream to the Vaman board.
7. Connect LEDs and switches to observe the multiplexer output.

## Output and Observation

When the select lines are changed, the output LED glows corresponding to the selected input line as per the truth table.

## Conclusion

The 4x1 multiplexer was successfully implemented on the Vaman FPGA board. The output matched the expected behavior as per the truth table. This experiment demonstrates how combinational logic can be implemented on FPGA hardware using Verilog HDL.

## Result

A 4x1 MUX was designed, simulated, and verified on the Vaman FPGA board using LEDs as output indicators.